

**ISTANBUL TECHNICAL UNIVERSITY**  
**COMPUTER ENGINEERING DEPARTMENT**

**BLG 222E**  
**COMPUTER ORGANIZATION**  
**PROJECT REPORT**

**Project** : 3  
**DATE** : 15.05.2019  
**GROUP NO** : 34

**GROUP MEMBERS:**

150170005 : SONER OZTURK  
150170062 : MEHMET FATIH YILDIRIM  
150170098 : SAHIN AKKAYA  
150170715 : MUSTAFA TEMURTAS

**SPRING 2019**

# Contents

FRONT COVER

CONTENTS

1	INTRODUCTION	1
2	Project	2
3	CONCLUSION	28

# 1 INTRODUCTION

In this project we design a hardware control unit which operates operations in given Figure1. We decided on which operations to do according to the 5 bit OPCODE in the instructions. In order to appropriate implementation Project2 has modified(which can be seen in Figure3) and Control Unit which control the inputs of components of the Basic Computer in Figure5 has implemented.

OPCODE (HEX)	SYMB	ADDRESSING MODE	DESCRIPTION
0x00	ADD	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} + \text{SRCREG2}$
0x01	SUB	N/A	$\text{DESTREG} \leftarrow \text{SRCREG2} - \text{SRCREG1}$
0x02	DEC	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} - 1$
0x03	INC	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1} + 1$
0x04	BRA	IM	$\text{PC} \leftarrow \text{Value}$
0x05	BEQ	IM	IF $Z=1$ THEN $\text{PC} \leftarrow \text{Value}$
0x06	BNE	IM	IF $Z=0$ THEN $\text{PC} \leftarrow \text{Value}$
0x07	LSL	N/A	$\text{DESTREG} \leftarrow \text{LSL SRCREG1}$
0x08	LSR	N/A	$\text{DESTREG} \leftarrow \text{LSR SRCREG1}$
0x09	LD	IM, D	$\text{Rx} \leftarrow \text{Value}$ (Value is described in Table 3)
0x0A	ST	D	$\text{Value} \leftarrow \text{Rx}$
0x0B	MOV	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1}$
0x0C	NOT	N/A	$\text{DESTREG} \leftarrow \text{NOT SRCREG1}$
0x0D	OR	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1 OR SRCREG2}$
0x0E	AND	N/A	$\text{DESTREG} \leftarrow \text{SRCREG1 AND SRCREG2}$

Figure 1: OPCODE field and symbols for operations and their descriptions

ADDRESSING MODE	MODE	SYMB	Value
0	Direct	D	$\text{M}[\text{AR}]$
1	Immediate	IM	ADDRESS Field

Figure 2: Addressing modes

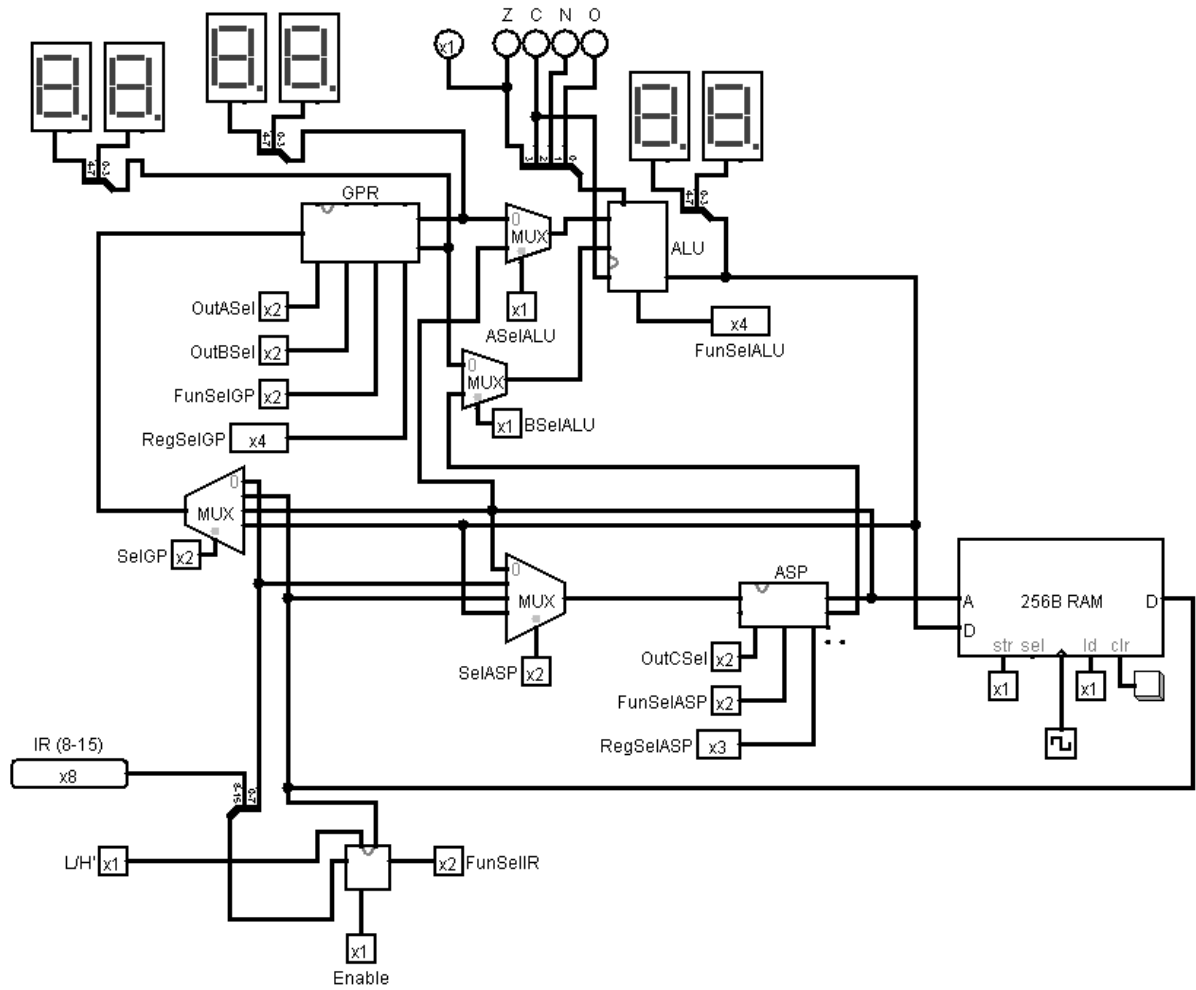


Figure 3: ALU System

## 2 Project

We design and implement a Control unit which can be seen in Figure 4 and Figure 5. Control unit provides necessary inputs during operations according to specific timing signal in that operation. In order to understand outputs of the Control Unit, we are going to analyze each operation below.



 


Figure 5: Control Unit

**Fetch and Decode:** this part is common in each of the operations from T0 to T3.

$$\text{IR}(8-15) = \text{M}[\text{PC}]$$

T0:

OutCSel: 10;

Read: 1;

L/H': 0;

Enable: 1;

FunSelIR: 00;

$$\text{PC} = \text{PC} + 1$$

T1:

RegSelASP: 001;

FunSelASP: 10;

$$\text{IR}(0-7) = \text{M}[\text{PC}]$$

T2:

OutCSel: 10;

Read: 1;

L/H': 1;

Enable: 1;

FunSelIR: 00;

$$\text{PC} = \text{PC} + 1$$

T3:

RegSelASP: 001;

FunSelASP: 10;

**After Fetch and Decode is done, each operation continues according to decoded Opcode.**

```
D0: DestReg = SrcReg1 + SrcReg2
IR10'IR7'IR4' (GPR = GPR + GPR)
DOT4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send B output of GPR to ALU as B
FunSelALU: 0101; // A + B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter
```

```
IR10'IR7'IR4 (GPR = GPR + ASP)
DOT4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutCSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send C output of ASP to ALU as B
FunSelALU: 0101; // A + B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter
```

```
IR10'IR7IR4' (GPR = ASP + GPR)
DOT4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send A output of GPR to ALU as B
FunSelALU: 0101; // A + B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
```



```

FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

IR10'IR7IR4 (GPR = ASP + ASP)
DOT4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0101; // A + B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

IR10IR7'IR4' (ASP = GPR + GPR)
DOT4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send B output of GPR to ALU as B
FunSelALU: 0101; // A + B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

IR10IR7'IR4 (ASP = GPR + ASP)
DOT4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutCSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send C output of ASP to ALU as B
FunSelALU: 0101; // A + B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers

```

SC = 0; // Done, Reset the counter

IR10IR7IR4' (ASP = ASP + GPR)

DOT4:

OutCSel: IR(6,5); // Select SrcReg1

ASelALU: 1; // Send C output of ASP to ALU as A

OutBSel: IR(3,2); // Select SrcReg2

BSelALU: 0; // Send A output of GPR to ALU as B

FunSelALU: 0101; // A + B

SelASP: 11; // Send Output of ALU to ASP

RegSelASP: IR(9,8); //D- Select DestReg

FunSelASP: 00; // Load enabled registers

SC = 0; // Done, Reset the counter

IR10IR7IR4 (ASP = ASP + ASP)

DOT4:

OutCSel: IR(6,5); // Select SrcReg1

ASelALU: 1; // Send C output of ASP to ALU as A

OutDSel: IR(3,2); // Select SrcReg2

BSelALU: 1; // Send D output of ASP to ALU as B

FunSelALU: 0101; // A + B

SelASP: 11; // Send Output of ALU to ASP

RegSelASP: IR(9,8); //D- Select DestReg

FunSelASP: 00; // Load enabled registers

SC = 0; // Done, Reset the counter

D1: DestReg = SrcReg1 - SrcReg2

IR10'IR7'IR4' (GPR = GPR - GPR)

D1T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

OutBSel: IR(3,2); // Select SrcReg2

BSelALU: 0; // Send B output of GPR to ALU as B

FunSelALU: 0111; // A - B

SelGP: 11; // Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

```

FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

IR10'IR7'IR4 (GPR = GPR - ASP)
D1T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutCSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send C output of ASP to ALU as B
FunSelALU: 0111; // A - B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

IR10'IR7IR4' (GPR = ASP - GPR)
D1T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send A output of GPR to ALU as B
FunSelALU: 0111; // A - B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

IR10'IR7IR4 (GPR = ASP - ASP)
D1T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0111; // A - B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers

```

```

SC = 0; // Done, Reset the counter

IR10IR7'IR4' (ASP = GPR - GPR)
D1T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send B output of GPR to ALU as B
FunSelALU: 0111; // A - B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7'IR4 (ASP = GPR - ASP)
D1T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutCSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send C output of ASP to ALU as B
FunSelALU: 0111; // A - B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7IR4' (ASP = ASP - GPR)
D1T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send A output of GPR to ALU as B
FunSelALU: 0111; // A - B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7IR4 (ASP = ASP - ASP)
D1T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0111; // A - B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

D2: DestReg = SrcReg1  1
IR10'IR7' (GPR = GPR - 1)
D2T4:
OutASel: IR(6,5); //Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelGP: 11; //Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load SrcReg1
D2T5:
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 01; // Decrement DestReg
SC = 0; // Done, Reset the counter

```

```

IR10'IR7 (GPR = ASP - 1)
D2T4:
OutCSel: IR(6,5); // Select SrcReg1
SelGP: 10; // Send output of ASP to GPR
RegSelGP: IR(9,8) // D- Select DestReg
FunSelGP: 00; // Load SrcReg1
D2T5:
RegSelGP: IR(9,8) // D- Select DestReg
FunSelGP: 01; // Decrement DestReg

```

```

SC = 0; // Done, Reset the counter

IR10IR7' (ASP = GPR - 1)
D2T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelASP: 11; // Send output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load SrcReg1
D2T5:
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 01; // Decrement SrcReg1
SC = 0; // Done, Rest the counter

IR10IR7 (ASP = ASP - 1)
D2T4:
OutCSel: IR(6,5); // Select SrcReg1
SelASP: 01; // Send SrcReg1 to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load SrcReg1
D2T5:
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 01; // Decrement SrcReg1
SC = 0; // Done, Rest the counter

D3: DestReg = SrcReg1 + 1
IR10'IR7' (GPR = GPR + 1)
D3T4:
OutASel: IR(6,5); //Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelGP: 11; //Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load DestReg
D3T5:

```

```

RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 10; // Increment DestReg
SC = 0; // Done, Reset the counter

```

```

IR10'IR7 (GPR = ASP + 1)
D3T4:
OutCSel: IR(6,5); // Select SrcReg1
SelGP: 10; // Send output of ASP to GPR
RegSelGP: IR(9,8) // D- Select DestReg
FunSelGP: 00; // Load SrcReg1
D3T5:
RegSelGP: IR(9,8) // D- Select DestReg
FunSelGP: 10; // Increment DestReg
SC = 0; // Done, Reset the counter

```

```

IR10IR7' (ASP = GPR + 1)
D3T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelASP: 11; // Send output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load SrcReg1
D3T5:
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 10; // Increment SrcReg1
SC = 0; // Done, Rest the counter

```

```

IR10IR7 (ASP = ASP + 1)
D3T4:
OutCSel: IR(6,5); // Select SrcReg1
SelASP: 00; // Send SrcReg1 to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load SrcReg1
D3T5:
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 10; // Increment SrcReg1

```

SC = 0; // Done, Rest the counter

D4: PC = Value

D4T4:

SelASP: 01; // Send IR(0,7) to ASP

RegSelASP: 001; // Enable PC

FunSelASP: 00; // Load PC

SC = 0; // Done, Reset the counter

D5: If Z=1 then PC = Value

Z

D5T4:

SelASP: 01; // Send IR(0,7) to ASP

RegSelASP: 001; // Enable PC

FunSelASP: 00; // Load PC

SC = 0; // Done, Reset the counter

Z'

D5T4:

SC = 0; // Done, Reset the counter

D6: If Z=0 then PC = Value

Z'

D6T4:

SelASP: 01; // Send IR(0,7) to ASP

RegSelASP: 001; // Enable PC

FunSelASP: 00; // Load PC

SC = 0; // Done, Reset the counter

Z

D6T4:

SC = 0; // Done, Reset the counter

D7: DestReg = LSL SrcReg1

IR10'IR7' (GPR = LSL GPR)



D7T4:

```
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 1010; // LSL A
SelGP: 11; //Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load DestReg
SC = 0; // Done, Reset the counter
```

IR10'IR7 (GPR = LSL ASP)

D7T4:

```
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
FunSelALU: 1010; // LSL A
SelGP: 11; // Send output of ALU to GP
RegSelGP: IR(9,8); //D- Select Destreg
FunSelGP: 00; // Load DestReg
SC = 0; // Done, Reset the counter
```

IR10IR7' (ASP = LSL GPR)

D7T4:

```
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 1010; // LSL A
SelASP: 11; // Send output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load DestReg
SC = 0; // Done, Reset the counter
```

IR10IR7 (ASP = LSL ASP)

D7T4:

```
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
FunSelALU: 1010; // LSL A
SelASP: 11; // Send output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load DestReg
```

SC = 0; // Done, Reset the counter

D8: DestReg = LSR SrcReg1

IR10'IR7' (GPR = LSR GPR)

D8T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

FunSelALU: 1011; // LSR A

SelGP: 11; //Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

FunSelGP: 00; // Load DestReg

SC = 0; // Done, Reset the counter

IR10'IR7 (GPR = LSR ASP)

D8T4:

OutCSel: IR(6,5); // Select SrcReg1

ASelALU: 1; // Send C output of ASP to ALU as A

FunSelALU: 1011; // LSR A

SelGP: 11; // Send output of ALU to GP

RegSelGP: IR(9,8); //D- Select Destreg

FunSelGP: 00; // Load DestReg

SC = 0; // Done, Reset the counter

IR10IR7' (ASP = LSR GPR)

D8T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

FunSelALU: 1011; // LSR A

SelASP: 11; // Send output of ALU to ASP

RegSelASP: IR(9,8); //D- Select DestReg

FunSelASP: 00; // Load DestReg

SC = 0; // Done, Reset the counter

IR10IR7 (ASP = LSR ASP)

D8T4:

OutCSel: IR(6,5); // Select SrcReg1

```

ASelALU: 1; // Send C output of ASP to ALU as A
FunSelALU: 1011; // LSR A
SelASP: 11; // Send output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load DestReg
SC = 0; // Done, Reset the counter

```

```

D9: Rx = Value
IR8 (Immediate, value is equal to ADDRESS field)
D9T4:
SelGP: 00; // Send IR(0,7) to GPR
RegSelGP: IR(10,9) //D- Select Rx
FunSelGP: 00; // Load Rx
SC = 0; // Done, Reset the counter

```

```

IR8' (Direct, value is equal to M[AR])
D9T4:
SelASP: 01; // Send IR(0,7) to ASP
RegSelASP: 100; // Enable AR
FunSelASP: 00; // Load AR
OutCSel: 00; // Select AR
D9T5:
Read: 1;
SelGP: 01; // Send M[AR] to GPR
RegSelGP: IR(10,9) //D- Enable Rx
FunSelGP: 00; // Load Rx
SC = 0; // Done, Reset the counter

```

```

D10: Value = Rx
D10T4:
OutASel: IR(10,9); // Select Rx
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelASP: 01; // Send IR(0,7) to ASP
RegSelASP: 100; // Enable AR

```

```

FunSelASP: 00; // Load AR
OutCSel: 00; // Select AR
Write: 1;
SC = 0; // Done, Reset the counter

```

```

D11: DestReg = SrcReg1
IR10'IR7' (GPR = GPR)
D11T4:
OutASel: IR(6,5); //Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelGP: 11; //Send Output of ALU to GPR
RegSelGP: IR(9,8); //Select DestReg
FunSelGP: 00; // Load DestReg
SC = 0; // Done, Reset the counter

```

```

IR10'IR7 (GPR = ASP)
D11T4:
OutCSel: IR(6,5); // Select SrcReg1
SelGP: 10; // Send C output of ASP to GPR
RegSelGP: IR(9,8); // D- Select DestReg
FunSelGP: 00; // Load SrcReg1
SC = 0; // Done, Reset the counter

```

```

IR10IR7' (ASP = GPR)
D11T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0100; // A
SelASP: 11; // Send output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load SrcReg1
SC = 0; // Done, Reset the counter

```

```

IR10IR7 (ASP = ASP)
D11T4:

```

```

OutCSel: IR(6,5); // Select SrcReg1
SelASP: 00; // Send C output of ASP to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load SrcReg1
SC = 0; // Done, Reset the counter

```

```

D12: DestReg = NOT SrcReg1

```

```

IR10'IR7' (GPR = NOT GPR)

```

```

D12T4:

```

```

OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0010; // NOT A
SelGP: 11; // Send output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load DestReg
SC = 0; // Done, Reset the counter

```

```

IR10'IR7 (GPR = NOT ASP)

```

```

D12T4:

```

```

OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
FunSelALU: 0010; // NOT A
SelGP: 11; // Send output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load DestReg
SC = 0; // Done, Reset the counter

```

```

IR10IR7' (ASP = NOT GPR)

```

```

D12T4:

```

```

OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
FunSelALU: 0010; // NOT A
SelASP: 11; // Send output of ALU to GPR
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load DestReg

```

SC = 0; // Done, Reset the counter

IR10IR7 (ASP = NOT ASP)

D12T4:

OutCSel: IR(6,5); // Select SrcReg1

ASelALU: 1; // Send C output of ASP to ALU as A

FunSelALU: 0010; // NOT A

SelASP: 11; // Send output of ALU to GPR

RegSelASP: IR(9,8); //D- Select DestReg

FunSelASP: 00; // Load DestReg

SC = 0; // Done, Reset the counter

D13: DestReg = SrcReg1 OR SrcReg2

IR10'IR7'IR4' (GPR = GPR OR GPR)

D13T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

OutBSel: IR(3,2); //Select SrcReg2

BSelALU: 0; // Send B output of GPR to ALU as B

FunSelALU: 0001; // A OR B

SelGP: 11; // Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

FunSelGP: 00; // Load DestReg

SC = 0; // Done, Reset the counter

IR10'IR7'IR4 (GPR = GPR OR ASP)

D13T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

OutDSel: IR(3,2); // Select SrcReg2

BSelALU: 1; // Send D output of ASP to ALU as B

FunSelALU: 0001; // A OR B

SelGP: 11; // Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

FunSelGP: 00; // Load enabled registers

```

SC = 0; // Done, Reset the counter

IR10'IR7IR4' (GPR = ASP OR GPR)
D13T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutBSel: IR(3,2); //Select SrcReg2
BSelALU: 0; // Send B output of GPR to ALU as B
FunSelALU: 0001; // A OR B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10'IR7IR4 (GPR = ASP OR ASP)
D13T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0001; // A OR B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7'IR4' (ASP = GPR OR GPR)
D13T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutBSel: IR(3,2); //Select SrcReg2
BSelALU: 0; // Send B output of GPR to ALU as B
FunSelALU: 0001; // A OR B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load DestReg
SC = 0; // Done, Reset the counter

```

```

IR10IR7'IR4 (ASP = GPR OR ASP)
D13T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0001; // A OR B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7IR4' (ASP = ASP OR GPR)
D13T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send A output of GPR to ALU as B
FunSelALU: 0001; // A OR B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7IR4 (ASP = ASP OR ASP)
D13T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0001; // A OR B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```



D14: DestReg = SrcReg1 AND SrcReg2

IR10'IR7'IR4' (GPR = GPR AND GPR)

D14T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

OutBSel: IR(3,2); //Select SrcReg2

BSelALU: 0; // Send B output of GPR to ALU as B

FunSelALU: 0000; // A AND B

SelGP: 11; // Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

FunSelGP: 00; // Load DestReg

SC = 0; // Done, Reset the counter

IR10'IR7'IR4 (GPR = GPR AND ASP)

D14T4:

OutASel: IR(6,5); // Select SrcReg1

ASelALU: 0; // Send A output of GPR to ALU as A

OutDSel: IR(3,2); // Select SrcReg2

BSelALU: 1; // Send D output of ASP to ALU as B

FunSelALU: 0000; // A AND B

SelGP: 11; // Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

FunSelGP: 00; // Load enabled registers

SC = 0; // Done, Reset the counter

IR10'IR7IR4' (GPR = ASP AND GPR)

D14T4:

OutCSel: IR(6,5); // Select SrcReg1

ASelALU: 1; // Send C output of ASP to ALU as A

OutBSel: IR(3,2); //Select SrcReg2

BSelALU: 0; // Send B output of GPR to ALU as B

FunSelALU: 0000; // A AND B

SelGP: 11; // Send Output of ALU to GPR

RegSelGP: IR(9,8); //D- Select DestReg

FunSelGP: 00; // Load enabled registers

SC = 0; // Done, Reset the counter

```

IR10'IR7IR4 (GPR = ASP AND ASP)
D14T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0000; // A AND B
SelGP: 11; // Send Output of ALU to GPR
RegSelGP: IR(9,8); //D- Select DestReg
FunSelGP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7'IR4' (ASP = GPR AND GPR)
D14T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutBSel: IR(3,2); //Select SrcReg2
BSelALU: 0; // Send B output of GPR to ALU as B
FunSelALU: 0000; // A AND B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load DestReg
SC = 0; // Done, Reset the counter

```

```

IR10IR7'IR4 (ASP = GPR AND ASP)
D14T4:
OutASel: IR(6,5); // Select SrcReg1
ASelALU: 0; // Send A output of GPR to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0000; // A AND B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7IR4' (ASP = ASP AND GPR)
D14T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutBSel: IR(3,2); // Select SrcReg2
BSelALU: 0; // Send A output of GPR to ALU as B
FunSelALU: 0000; // A AND B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

```

IR10IR7IR4 (ASP = ASP AND ASP)
D14T4:
OutCSel: IR(6,5); // Select SrcReg1
ASelALU: 1; // Send C output of ASP to ALU as A
OutDSel: IR(3,2); // Select SrcReg2
BSelALU: 1; // Send D output of ASP to ALU as B
FunSelALU: 0000; // A AND B
SelASP: 11; // Send Output of ALU to ASP
RegSelASP: IR(9,8); //D- Select DestReg
FunSelASP: 00; // Load enabled registers
SC = 0; // Done, Reset the counter

```

## Simplified version of logical expressions of the control unit components;

OutASel:

IR(10-9): D10T4

IR(6-5): T4IR7'(D0 + D1 + D2 + D3 + D7 + D8 + D11 + D12 + D13 + D14)

OutBSel:

IR(3-2): T4IR4'(D0 + D1 + D13 + D14)

OutCSel:

00: T4(D10 + D9IR8)

10: T0 + T2

IR(6-5): T4IR7(D0 + D1 + D2 + D3 + D7 + D8 + D11 + D12 + D13 + D14)

IR(3-2): T4IR4(IR7'(D0 + D1))

OutDSel:

IR(3-2): T4IR4IR7(D0 + D1) + T4IR4(D13 + D14)

FunSelASP:

00: T4IR10(D0+D1+D2+D3+D11+D12+D13+D14+D7+D8) + T4(D4 + D5Z + D6Z' + D9IR8' + D10)

01: D2IR10T5

10: T1 + T3 + (D3IR10T5)

FunSelGP:

00: T4IR10'(D0+D1+D2+D3+D7+D8+D11+D12+D13+D14) + D9T4IR8 + D9T5IR8'

01: D2T5IR10

10: D3T5IR10'

RegSelASP:

IR(9,8): T4IR10(D0+D1+D2+D3+D7+D8+D11+D12+D13+D14) + T5IR10(D2+D3)

001: T1 + T3 + T4D4 + ZT4D5 + ZT4D6

100: T4D10

RegSelGP:

IR(10-9):  $T4D9(IR8 + IR8')$

IR(9-8):  $T5IR10'(D2 + D3) + T4IR10'(D0+D1+D2+D3+D11+D12+D13+D14+IR7'(D7+D8))$

ASelAlu:

0:  $T4IR7'(D0+D1+D2+D3+D7+D8+D11+D12+D13+D14) + D10T4$

1:  $T4IR7(D0+D1+D7+D8+D12+D13+D14)$

BSelAlu:

0:  $T4IR4'(D0 + D1 + D13 + D14)$

1:  $T4IR4(D0 + D1 + D13 + D14)$

FunSelAlu:

0000:  $D14T4$

0001:  $D13T4$

0010:  $D12T4$

0100:  $T4(IR7'(D2 + D3 + D11) + D10)$

0111:  $D1T4$

0101:  $D0T4$

1010:  $D7T4$

1011:  $D8T4$

SelGP:

00:  $D9IR8T4$

01:  $D9T5IR8'$

10:  $IR7T4IR10'(D11 + D2 + D3)$

11:  $T4IR10'(D0 + D1 + IR7'(D2 + D3 + D11) + D7 + D8 + D12 + D13 + D14)$

SelASP:

00:  $T4IR10IR7(D2+D3+D11)$

01:  $T4(D4 + D10 + D5Z D6Z')$

11:  $D0 + D1 + D7 + D8 + D12 + D13 + D14 + IR7'(D2 + D3 + D11)$

SC:

$T4(D0 + D1 + D4 + D5 + D6 + D7 + D8 + D9 + D10 + D11 + D12 + D13 + D14) +$

$T5(D2 + D3 + D9IR8')$

Read:

1: T0 + T2 + T4D9IR8'

Write:

1: T4D10

### 3 CONCLUSION

In this project, we designed a hardware control unit that controls the basic computer we made in the second project. We also made some changes on the basic computer to do the project. While we were designing this project, we gained experience on hard-wired implementing of basic computer and processing operations.